

Total number of printed pages-7

3 (Sem-4/CBCS) PHY HC 3

2024

PHYSICS

(Honours Core)

Paper : PHY-HC-4036

(Analog Systems and Applications)

Full Marks : 60

Time : Three hours

**The figures in the margin indicate
full marks for the questions.**

1. Answer the following questions as directed :

1×7=7

- (i) For a PN junction, barrier potential _____ with increase in junction temperature. (Fill in the blank)

Contd.

- (ii) Zener breakdown occurs in heavily-doped junction, whereas avalanche breakdown occurs in lightly-doped ones. *(Write True or False)*
- (iii) LEDs emit light only when _____ biased. *(Fill in the blank)*
- (iv) The leakage currents in a transistor are due to _____ carriers. *(Fill in the blank)*
- (v) Multistage amplifiers are used in order to achieve greater
- (a) voltage gain
 - (b) power gain
 - (c) frequency response
 - (d) All of the above
- (Choose the correct option)*
- (vi) For class A operation of an amplifier, Q-point is located at the _____ of the load line. *(Fill in the blank)*

(vii) The analog to digital converter are employed in

(a) voltmeter

(b) wattmeter

(c) energy meter

(d) digital multimeter

(Choose the correct option)

2. Give short answer of the following questions :

2×4=8

(i) Define ripple as referred to in a rectifier circuit. What is meant by filter ?

(ii) What does common-mode rejection ratio (CMRR) of a differential amplifier physically signify ? Express CMRR in dB form.

(iii) Draw a fixed-bias circuit of a transistor.

(iv) Explain the need for regulated power supply.

3. Answer the following questions : **(any three)**

5×3=15

(i) The signals applied to the inverting and non-inverting terminals of a differential amplifier are -0.40 mV and -0.42 mV respectively. If the differential gain and the CMRR are 10^5 and 80 dB respectively, find the total output voltage. 5

(ii) Explain with circuit diagram how an op-amp can be used as an adder or summing amplifier. 5

(iii) Define common-base current amplification factor (α) and common-emitter current amplification factor (β). Derive the relation between them. 2+3=5

(iv) Using h-parameter, draw the two-generator form of the equivalent circuit. Define the four h-parameters. Why are the h-parameters very useful for circuit analysis? 2+2+1=5

(v) Write short notes on : $2\frac{1}{2}+2\frac{1}{2}=5$

(a) Zener diode

(b) Solar cell

4. Answer the following questions : **(any three)**

$10 \times 3 = 30$

(i) Sketch the output characteristics of a transistor in its CB mode. Explain the active, cut-off and saturation regions.

A transistor in a CB mode, with $\alpha = 0.98$ gives a reverse saturation current $I_{CBO} = 12 \mu A$. When used in a CE mode, it gives the base current of $0.2 mA$. Calculate its total collector current in a CE mode. $6+4=10$

(ii) Draw circuit diagram of a full-wave bridge rectifier and explain its operation. What are its ripple factor, maximum rectification efficiency and peak inverse voltage? $7+3=10$

- (iii) Explain the term 'feedback'. What are positive and negative feedbacks? Derive an expression for the voltage gain of an amplifier with feedback. Give the advantages of negative feedback.

$$2+2+3+3=10$$

- (iv) Draw a circuit diagram of a single-stage CE transistor amplifier as well as its equivalent circuit. Derive the expressions for current gain and voltage gain of such an amplifier.

$$4+6=10$$

- (v) With the help of a neat diagram, explain the working of a weighted resistor DAC. What are its advantages and disadvantages? Write any two major applications of D/A converters.

$$4+(2+2)+2=10$$

(vi) Write short notes on : **(any two)**

5×2=10

(a) RC phase-shift oscillator

(b) Hartley oscillator

(c) Logarithmic amplifier using
OPAMP

